


# ELECTRIC CIRCUITS

## 1. Recap the basics:


Ⓥ — voltmeter

Ⓐ — ammeter

⊗ — bulb

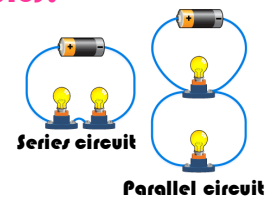
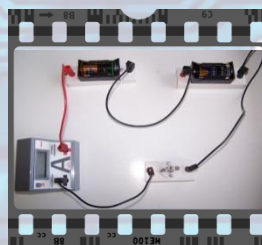
## 2. Set up each experiment for practice



## 3. Collect your equipment tray



## 4. Build these circuits in the above space. Find the voltage and current values.

## 5. Ask for extension tasks.

